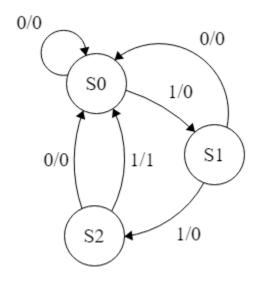
3.

A)

Kod Mealy automata izlaz ovisi samo o trenutnom stanju I o ulazu



S0 = 00(pocetno stanje) , S1 = 01, S2 = 10

		1			
Trenutna Stanja		Ulaz	Iduca Stanja		izlaz
Q1	Q0	Χ	Q1_next	Q0_next	Υ
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	0	1
1	1	0	Х	Х	Х
1	1	1	х	х	Х

Za Q1next:

	C'	С
Q1'Q0'	0	0
Q1'Q0	0	
Q1Q0	X	x x
Q1Q0'	0	0

Q1next=Q0X

Za Q0next:

	C'	С
Q1'Q0'	0	
Q1'Q0	0	0
Q1Q0	X	X
Q1Q0'	0	0

Q0next=Q1'Q0'X

Za Y:

	C'	С
Q1'Q0'	0	0
Q1'Q0	0	0
Q1Q0	X	x X
Q1Q0'	0	1

Y=Q1X

Slijedi da nasa shema za mealy automat izgleda:

